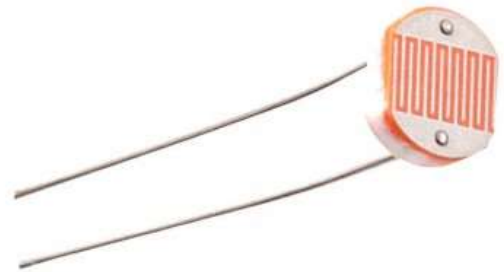


# Interfacing of LDR sensor



# Light Dependent Resistor

An **LDR** is a component that has a (variable) resistance that changes with the light intensity that falls upon it. This allows them to be used in light **sensing** circuits. A Light Dependent **Resistor** (**LDR**) or a photo **resistor** is a device whose resistivity is a **function** of the incident electromagnetic radiation. Hence, they are light sensitive devices. They are also called as photo conductors, photo conductive cells or simply photocells.



# Working of LDR sensor


Reading a photo sensor with the Arduino Mega:

- We will use a LDR and a resistor together in series. An LDR is simply a device that changes resistance based on ambient light. The brighter the light, the lower the resistance, the dimmer the light, the higher the resistance.
- When there is no light, LDR will offer high resistance and less current flows through the resistor and voltage across resistor will be less near to GND.
- When light falls on LDR, its resistance decreases and current flow through it increases. Then voltage across the resistor increases and pin 22 gets a HIGH signal.

# Components required

- Arduino mega
- LDR sensor
- LED
- Resistor (10k)
- Breadboard
- Jumper wires

# Connection Diagram

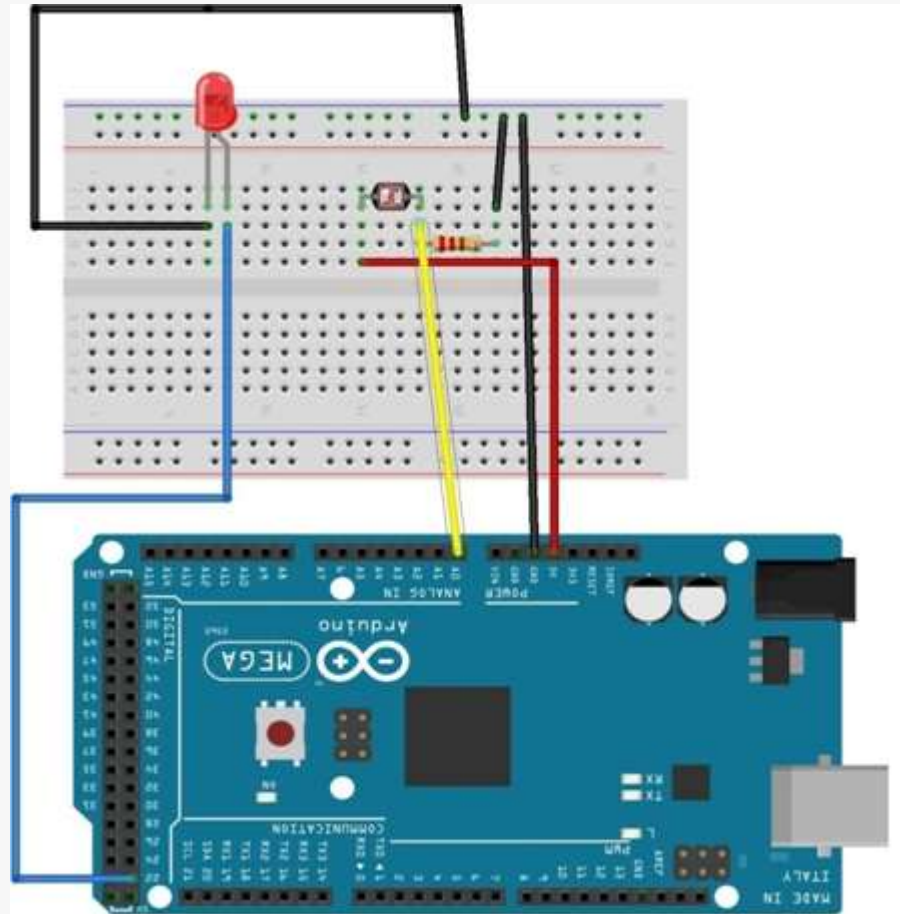

# Connections

1. Connect 1<sup>st</sup> pin of LDR sensor with Ao pin of Arduino.
2. Connect resistor(10k) with 1<sup>st</sup> pin of LDR sensor.
3. Then connect resistor's another end with GND pin of Arduino
4. Connect 2<sup>nd</sup> pin of LDR sensor with (+5V) of Arduino.
5. Connect LED's positive to 22 pin of Arduino and LED's negative with GND of Arduino.



**Project Link :** <https://youtu.be/Cc8CTB25uyU>