
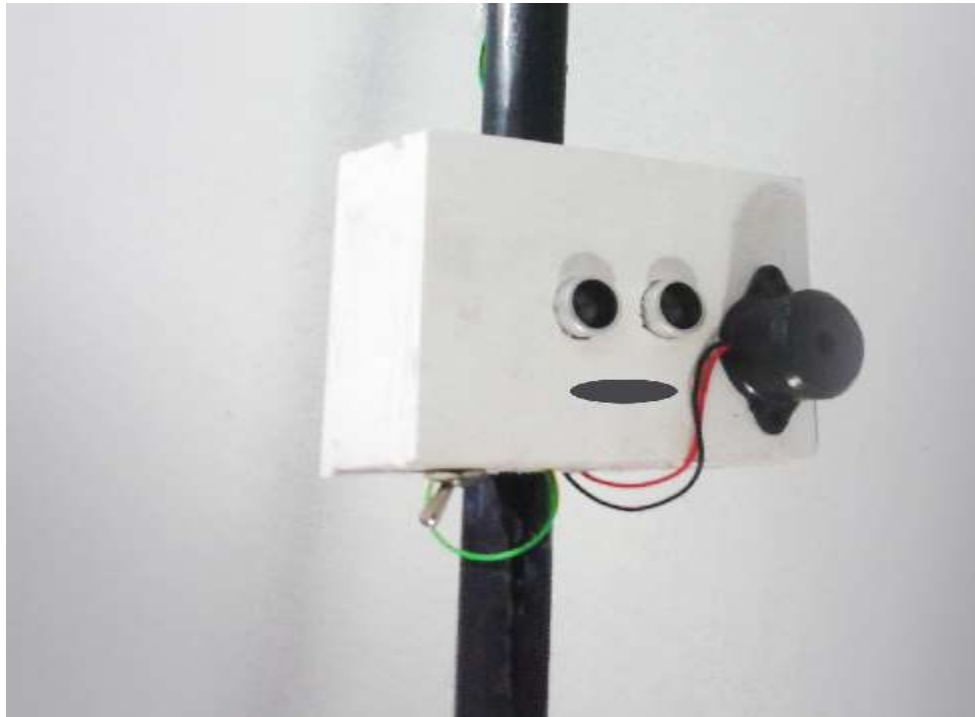


Blind Stick Project

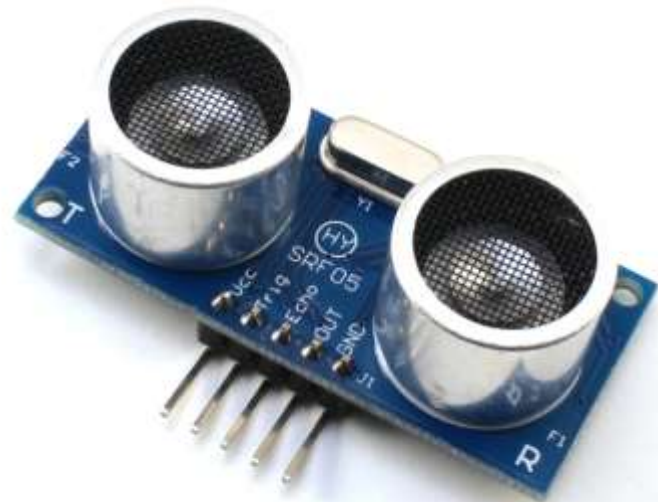

Ultrasonic Sensor HC-SR04



An **ultrasonic sensor** is an instrument that measures the distance to an object using **ultrasonic** sound waves. An **ultrasonic sensor** uses a **transducer** to send and receive **ultrasonic** pulses that relay back information about an object's proximity.



Working principle of Ultrasonic Sensor

- **Ultrasonic sensors work** by emitting sound waves at a frequency too high for humans to hear. Then they wait for the sound to be reflected back, calculating distance based on the time required. This is similar to how radar measures the time it takes a radio wave to return after hitting an object.
- The HC-SR04 offers excellent non-contact range detection with high accuracy and stable readings in an easy-to-use package from 2 cm to 400 cm or 1" to 13 feet.

Working Diagram

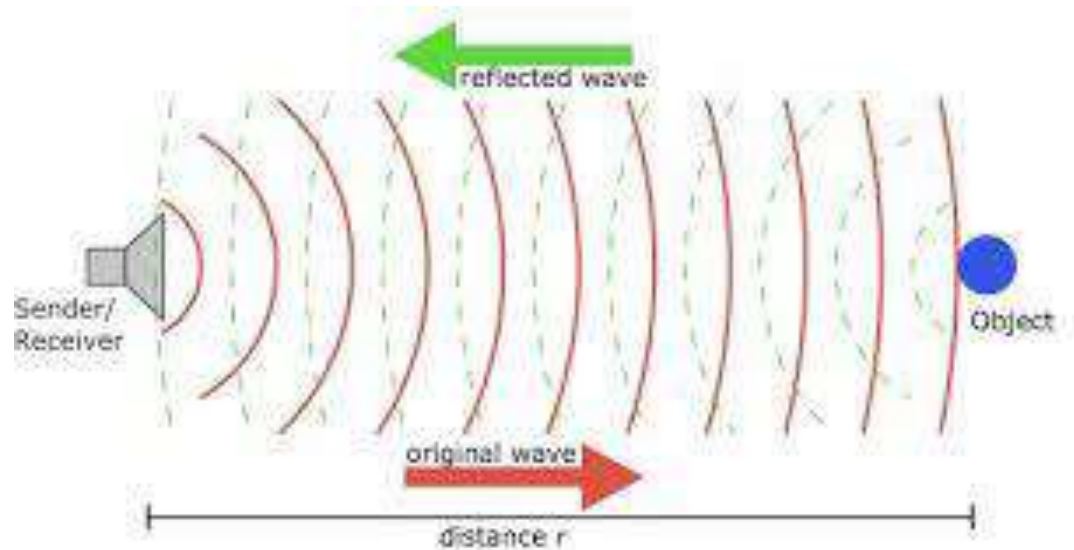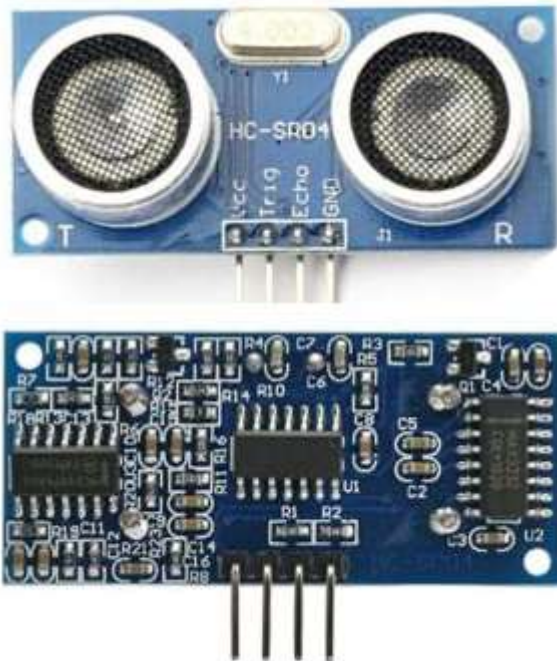

Working of project

- There are two openings in Ultrasonic sensor first is transmitter (or Trigger) and second is receiver (or Echo).
- Ultrasonic sensor sends high frequency pulses, these pulses reflect from object and take as Echo, time between echo and Trig is measured by the microcontroller or Arduino which is directly proportional to distance.
- The speed of sound is 341 meter per second in the air, and the distance between sensor and object is equal to time multiplied by speed of sound divided by two.


$$\text{Distance} = (\text{Time} * \text{Speed Of Sound}) \div 2$$

- After the distance measurement, Arduino makes a beep format using buzzer, when distance is high, frequency of beep is decreased and beep frequency is increased when distance is low.

Components Required

- Arduino Nano
- Ultrasonic Sensor HC-SR04
- Buzzer
- Breadboard
- Jumper wires

Connection Diagram

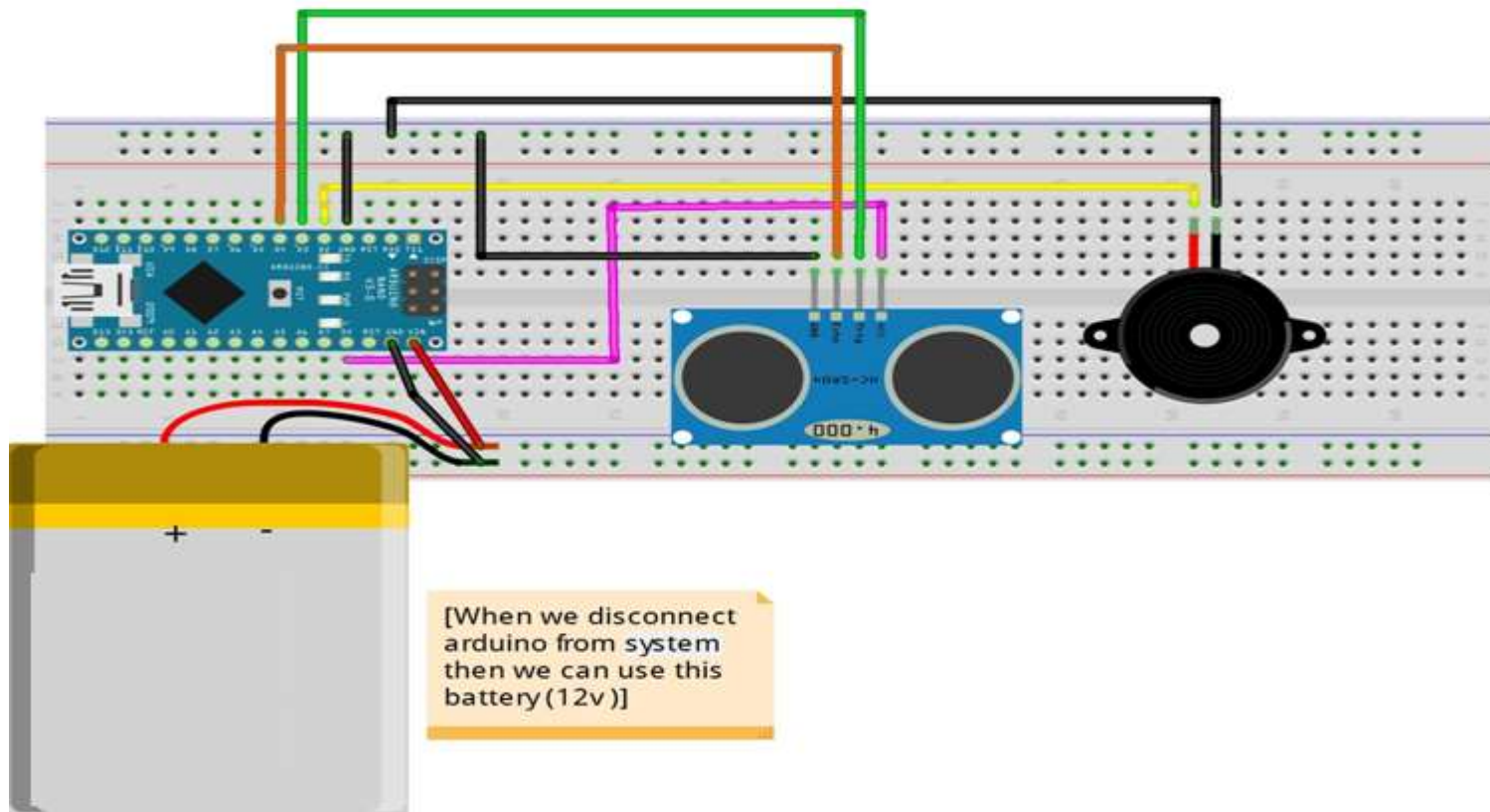

Connections

1. Connect **Trig** pin of Ultrasonic sensor with **D3** pin of Arduino Nano.
2. Connect **Echo** pin of Ultrasonic sensor with **D4** pin of Arduino Nano.
3. Connect **Vcc** pin of Ultrasonic sensor with **5V** of Arduino Nano.
4. Connect **GND** pin of Ultrasonic sensor with **GND** of Arduino Nano.
5. Connect positive pin of buzzer with **D2** pin of Arduino Nano and negative pin with **GND** pin of Arduino Nano.
6. After uploading the code in Arduino, remove Arduino cable and connect **12V** li-ion battery with Arduino Nano.

Project Link: <https://youtu.be/bltl44lYJBI>